

EEE 122

Lab report 01

Experiment name: To design and  
implement a half-wave  
rectifier circuit.

Name: Md. Sharafat Karim

Roll : 2102024

Reg : 10151

Level-01, Sem-02



ID 2102024

Experiment name: To design and implement a half-wave rectifier circuit.

### Theory:

During half-wave rectification, the rectifier conducts current only during the positive half-cycles of input a.c. supply. The negative half-cycles of a.c. supply are suppressed i.e. during negative half-cycles no current is conducted and hence no voltage appears across the load.

### Operation:

The a.c. voltage across the secondary winding AB changes polarities after every half-cycle. During the positive half-cycle of input a.c. voltage, end A becomes positive w.r.t. end B. This makes the diode forward biased and hence it conducts current.

During the negative half-cycle, end A is

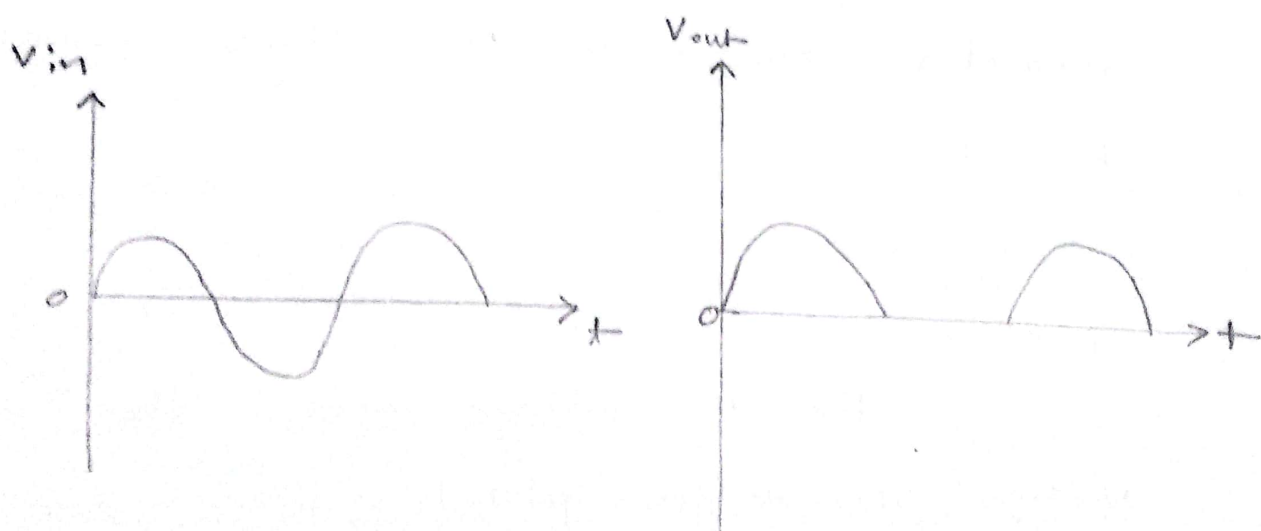
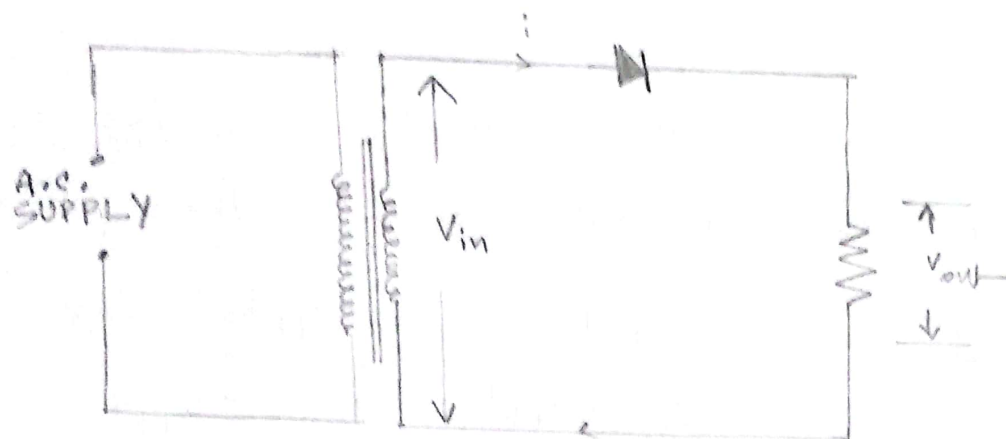


Figure: Half wave rectifier

negative w.r.t. end B. Under this condition the diode is reverse biased and it conducts no current. Therefore, current flows through the diode during positive half-cycles of input ac. voltage only. And also it is blocked in the negative half cycle. In this way current flows in the same direction.

#### Apparatus :

Function generator, regulated power supply, resistor, diode, Bread board, Oscilloscope, connecting wires, diodes, multimeter, transformer and capacitors as required.

#### Procedure :

- 1) Connect the circuit like the diagram
- 2) Give the input signal as required.





- 3) Switch on the power supply
- 4) Measure the output voltage and current using a multimeter or oscilloscope.
- 5) Record the obtained data including voltage ripple, output voltage and efficiency.
- 6) Analyze the performance of the half wave rectifier circuit.
- 7) Take necessary steps to remove the AC components from the output through ripple filter circuit.

### Calculations:

Here, AC power input,

$$P_{ac} = I_{rms}^2 (r_f + R_L)$$

D.C. power output,

$$P_{dc} = (I_m / \pi)^2 \times R_L$$

$$\therefore \text{Rectifier efficiency} = \frac{P_{dc}}{P_{ac}} = \frac{(I_m / \pi)^2 \times R_L}{(I_m / 2)^2 \times (r_f + R_L)}$$

$$= 0.406 \text{ or } 40.6\%$$





$$\therefore \text{ripple factor} = \sqrt{\left(\frac{I_m/2}{I_m/\pi}\right)^2 - 1}$$
$$= 1.21$$

### Discussion:

- 1) Diodes should be placed carefully with proper direction.
- 2) Resistance should be measured beforehand.
- 3) Proper thermal management is required.
- 4) Half wave rectifiers produce DC with ripple voltage. Filter circuits are required for a smoother output.



Lab report 02 (EEE 122)

Experiment: To design and implement  
a full wave bridge rectifier  
circuit.

Submitted by:

Name: Md. Sharafat Karim

Roll : 2102024

Reg : 10151

Level - 01, Sem - 02



ID 2102024

Experiment name: To design and implement a full wave bridge rectifier circuit.

### Theory:

The conversion of AC into DC is called rectification. Electronic devices can convert it implicitly. The bridge is composed of four diodes in a circle shape. During the positive half cycle, the end of the secondary winding becomes positive and other end negative.

This makes diodes  $D_1$  and  $D_3$  forward biased while diodes  $D_2$  and  $D_4$  are reverse biased. Therefore only diodes  $D_1$  and  $D_3$  conduct.

During the negative half-cycle of secondary voltage, end becomes negative and the other end positive. This makes  $D_2$  and  $D_4$  forward biased whereas diodes  $D_1$  and  $D_3$  are reverse biased. Therefore in this case, only  $D_2$  and  $D_4$  will conduct.



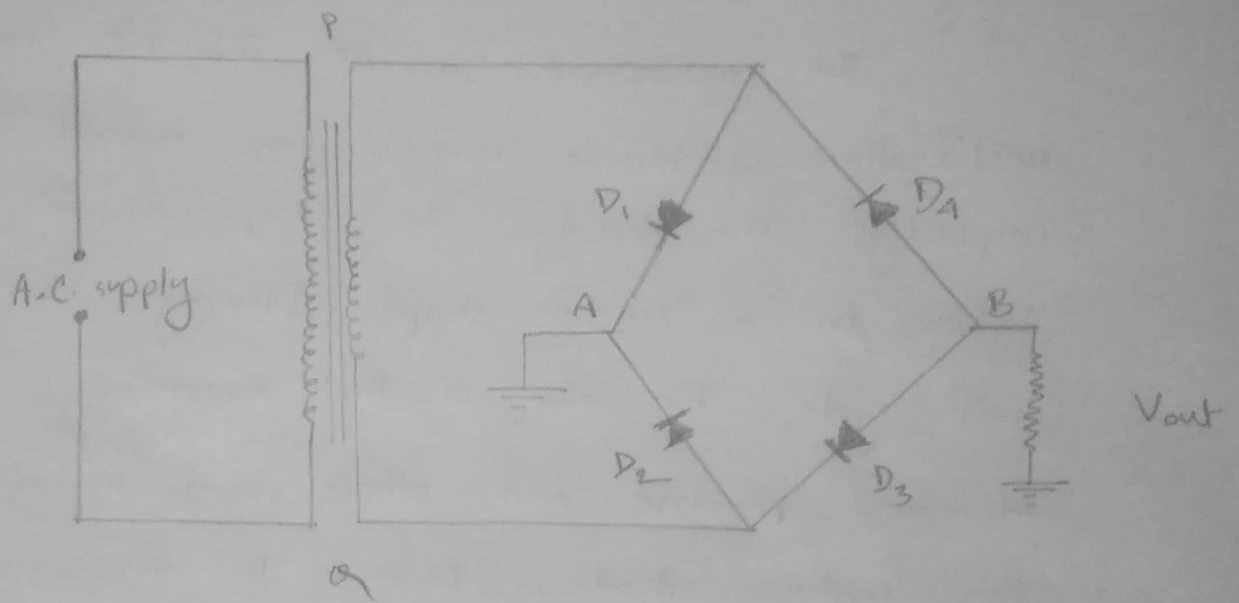


Figure: Full wave rectifier

### Apparatus :

Bread board, Oscilloscope, Resistance, Connecting wires, diodes, multimeter, capacitors, transformer and regulated power supply.

### Procedure :

- 1) Connect the circuit like the diagram
- 2) Give the input signal as required
- 3) Switch on the power supply
- 4) Measure the output voltage and current using a multimeter or oscilloscope.
- 5) Record the obtained data including voltage ripple, output voltage and efficiency.
- 6) Analyze the performance of the full-wave rectifier circuit.
- 7) Check ripple-factors. Also take necessary steps to decrease the AC amount from the output.

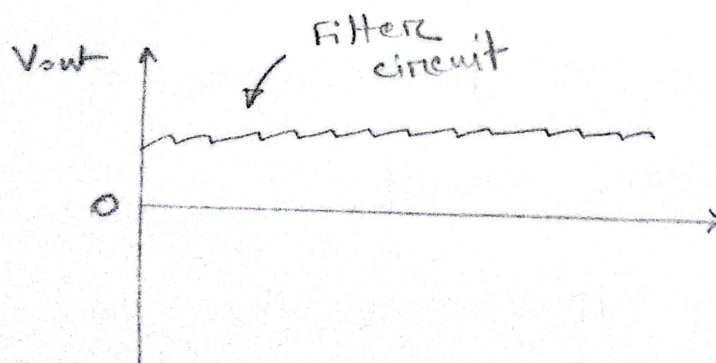
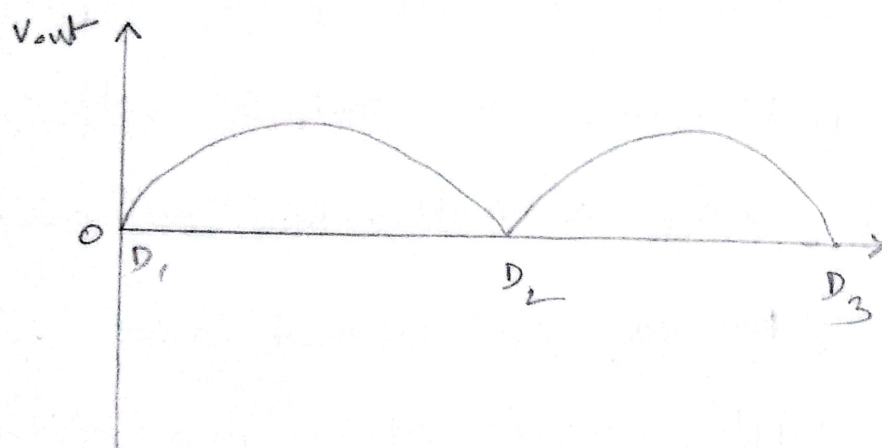
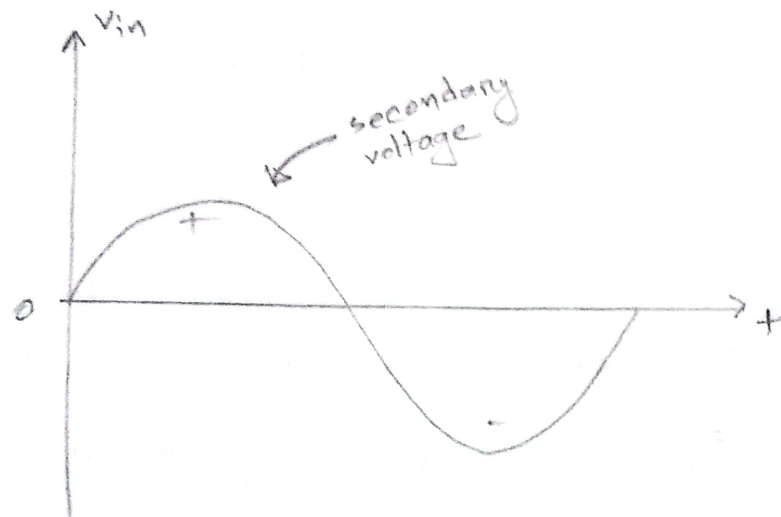


Figure: Graph of full-wave rectifier

### Results:

1. Output waveform frequency = 1 kHz

2. Ripple factor

$$r = \sqrt{\left(\frac{I_m/\sqrt{2}}{2I_m/\pi}\right)^2 - 1}$$

$$= 0.48$$

3. Efficiency

$$\eta = \frac{\text{dc power output}}{\text{ac power input}}$$

$$= \frac{(2I_m/\pi)^2 R_L}{(I_m/\sqrt{2})^2 (R_f + R_L)}$$

$$= 0.812 \text{ or } 81.2\%$$

### Discussion:

1) Four diodes should be placed carefully with proper direction.

2) Resistance should be measured beforehand.

3) Proper thermal management is required

4) Proper grounding is required in the breadboard.

